

ELECTRIC CURRENT

Rate of flow of Charge $I = \frac{dq}{dt}$

S.I. Unit Ampere (A) Coulomb/ Second


Instantaneous, $I_{ins} = \frac{dq}{dt}$

Average, $I_{av} = \frac{q}{t}$

Ohm's Law

- At constant temperature current passing through metals or conductors is directly proportional to the potential difference applied across them.
- $I \propto V \Rightarrow V = IR$; (R-electric resistance)
- Substances which Obey Ohm's law called Ohmic and that do not obey called non-ohmic substances.

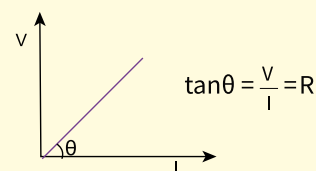The slope of V-I plot for Ohmic substance



Drift Velocity


Drift velocity is defined as the velocity with which the free electrons get drifted towards the positive terminal under the effect of the applied external electric field.

$$V_d = \frac{qE}{m} \tau$$

Relation between Drift velocity and current

$$i = neAV_d = \frac{ne^2 A \tau E}{m}$$
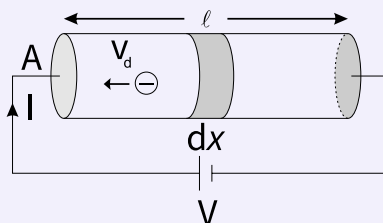
$$= neA \mu_e E = neA \mu_e \frac{V}{\ell}$$




CURRENT ELECTRICITY

Current density (J)

Current per unit cross-section area perpendicular to current flow.

$$J = \frac{I}{A} = \frac{E}{\rho}$$

Resistance

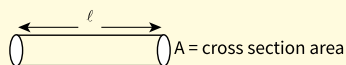

The property due to which body opposes the flow of current through it, is known as resistance.

$$R = \frac{\rho \ell}{A}$$

S.I unit of Resistivity: ohm (Ω)

Factors affecting resistivity:

- Nature of material
- Temperature.

Relation between resistivity and temperature

$$\rho_t = \rho_i [1 + \alpha (t_f - t_i)]$$

Grouping of Resistance

Series grouping of resistance

- Equivalent resistance, $R_s = R_1 + R_2 + R_3, \dots$
- Diagram showing three resistors R_1, R_2, R_3 connected in series with current I flowing through them.
- Current flow through each resistance is same.
- Potential difference, $V \propto R$

Parallel grouping of resistance

- Equivalent resistance,
- $$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$
- Diagram showing three resistors R_1, R_2, R_3 connected in parallel.
- Potential difference across each resistance same current distribution, in each resistance, $I \propto \frac{1}{R}$

Some Important Formula

- After stretching length of wire increases by n times then resistance will increase by n^2 times i.e.,
- If radius be reduced $\frac{1}{n}$ to times then area of cross-section decreases $\frac{1}{n^2}$ time so the resistance become n^4 times i.e., $R_2 = n^4 R_1$

Conductivity (σ)

$$\sigma = \frac{1}{\text{Resistivity}} = \frac{1}{\rho}$$

$$\text{Unit} = \frac{1}{\Omega \text{m}} = \frac{1}{\text{ohm} \times \text{m}} \text{ or } \frac{\text{mho}}{\text{m}}$$

Electric Energy and Power

Heat energy developed across resistor $H = I^2 RT$

$$\text{Power, } P = VI = I^2 R = \frac{V^2}{R}$$

In parallel, $P = P_1 + P_2$

$$\text{In series, } P = \frac{P_1 P_2}{P_1 + P_2}$$

Conductance

$$C = \frac{1}{\text{Resistance}} = \frac{1}{R}$$

Unit is mho (Ω^{-1})

Grouping of cells

Cells in series

Current in the circuits, $I = \frac{n\varepsilon}{R + nr}$

Cells in parallel


Current in the circuit, $I = \frac{\varepsilon}{R + \frac{r}{m}}$

Cells in mixed grouping


The current in the circuit,

$$I = \frac{n\varepsilon}{\frac{nr}{m} + R}$$

When cell is discharging

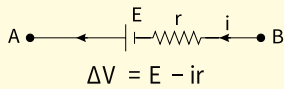

When cell is charging

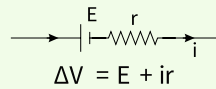

When cell is in an open circuit

$R = \infty$
 $I = \frac{E}{R+r} = 0$ and $V = E$


When cell is short circuited

$R = 0$ and $I = \frac{-E}{R+r}$ and $V = IR = 0$

Kirchhoff's laws


1st law/ Junction law

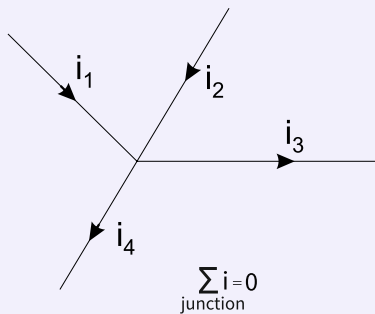- Sum of the incoming currents is equal to sum of the outgoing currents at any junction.
- Based on law of conservation of charge.




2nd law/loop rule

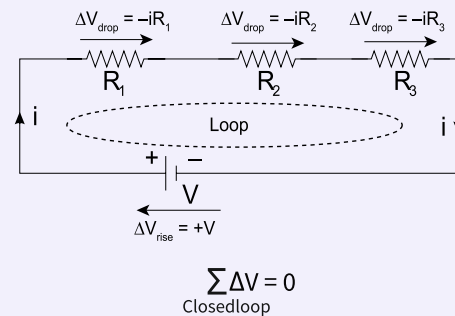- The algebraic sum of the potential differences in any loop (including those associated with emf's and those of resistive elements), must equal zero.
- Based on law of conservation of energy.



Wheatstone Bridge

Balanced Condition of Wheatstone bridge

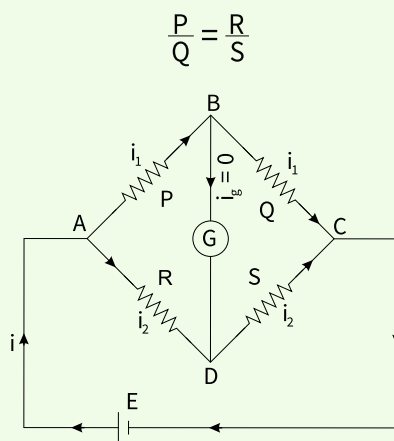

Metre bridge

Based on Wheatstone bridge

$$\frac{P}{Q} = \frac{R}{S} = \frac{\ell}{100 - \ell}$$

